



Automotive Electrics Basics

Last updated 15-Dec-2023

If you find the information here useful, you may like to make a small contribution to help offset the costs of providing it. Thank you.



Electricity probably causes the most problems for classic car owners, perhaps because usually you don't see, hear, feel or smell it until something starts going wrong! But electricity - unlike mechanical systems - operates to strict laws, so understanding the basics of electrical circuits should help you to work out what is going wrong when something doesn't work as it should. These words are written by someone with primarily MGB knowledge, but hopefully will be of use to owners of earlier MGs and other classics.

Part 1 - Terminology

[Battery](#) [Voltage](#) [Current](#) [Circuit](#) [Resistance](#) [Ohm's Law](#) [Watts/Power](#) [Earth/Ground](#) [Live and Earth terminals](#)
[Polarity](#) [Open-circuit](#) [Short-circuit](#) [Fuse](#) [Series Circuit](#) [Parallel Circuit](#)

[Click here](#) for Part 2 - Electrical systems, typical faults, causes, symptoms, and diagnostic techniques

Battery: The initial power source for the electrical systems in a car. Without a working battery you cannot start the engine by normal means, and if one is not even installed and connected you should not attempt to do so by other means as that can cause damage.

The battery normally contains a large amount of energy and as such **extreme care** needs to be taken to avoid metal objects coming into contact with the terminal posts and connectors. Batteries must be securely clamped down to prevent them bouncing around and the terminals coming into contact with metal parts, of particular risk in cars like the MGB with a metal cover just above the battery. Anything that bridges the battery terminals together will generate a large spark which can ignite battery gases, get literally red hot and weld things together. These safety aspects are covered in the [detailed technical section on batteries](#).

Car batteries are capable of delivering a very high amount of energy for a short period of time as when starting the engine, as well as a much smaller amount of energy for a long period of time e.g. parked with the lights on. One terminal of the battery is known as the 'positive' or +ve terminal, the other is the 'negative' or -ve terminal.


Some sources purporting to give basic automotive electrical information also go into how a battery works i.e. the chemical reactions involved, current flow and electron flow, and which flows from positive to negative and which from negative to positive. But that's all irrelevant for fault diagnosis purposes and may just confuse, Google it if you are interested.

Voltage: This is the force of electricity coming from the source expressed as a number of Volts and given the symbol 'V'. It is often likened to the pressure of water forcing water out of a hosepipe, which at the very simplest level is not unreasonable. But further comparisons which some explanations of electrical circuits are fond of introducing such as reducing the size of the nozzle making the jet of water squirt further, are irrelevant as there is no functional equivalent in

electricity. Voltage measurements are the single most useful thing in diagnosing electrical problems.

Current: This is the volume of energy passing through wiring and circuits, expressed as a number of Amps and given the symbol 'I'. The greater the rate of movement through the wire, the greater the number of amps. Another loose comparison with water can be made - it is like the speed of water coming out of the garden hose. And just as in a water system you need a large pipe in order to deliver a large volume of water, in electrical circuits you need a large i.e. thick cable to deliver a high current. Electrical systems in the vehicles considered here are 'direct current' or DC, unlike most house systems which use 'alternating current' or AC. There are good reasons for the difference, and why cars typically use 12 volt systems and houses typically use 240 volt or 120 volt systems, but there is no need to go into that here, Google it if you are interested. With a couple of exceptions the need for current measurements is rare in diagnosing electrical problems, and it can be hazardous.


Circuit:

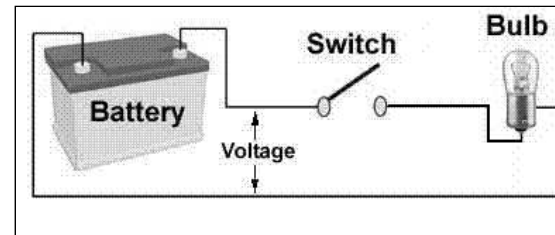

Electrical systems can only work when there is continuous path or 'circuit' for current to flow from a power source, to a component, with a return path back to the power source. Circuits typically consist of a power source such as a battery, a component that is going to be powered such as a light bulb, wiring to

connect the source to the component, and a switch so that the component can be turned on and off. The same current flows through all the components in a series circuit.


Resistance:

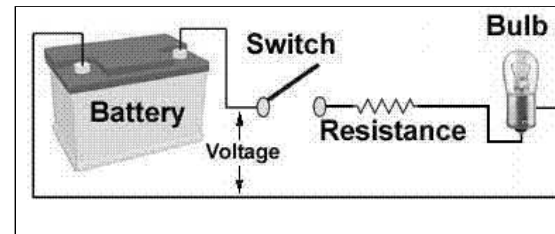

Resistance, as its name implies, 'resists' or restricts the amount of current that can flow in a circuit, expressed as a number of Ohms and given the symbol 'R'. And - in the last comparison with water and hoses - it could be thought of as a kink in that garden hose reducing the volume of water that can flow. The

higher the resistance is, the lower current that can flow in the circuit. As the current reduces then so the voltage that reaches the bulb (for example) also reduces, and the bulb will not glow as brightly. Unwanted resistance from bad connections is probably the biggest cause of problems in classic electrics.

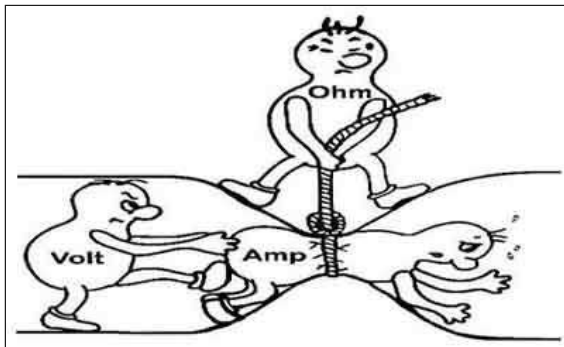So to put voltage, current and resistance into context, the voltage is trying to push a current through a circuit, but the resistance is trying to restrict how much current can flow in a circuit.




Ohm's Law:

Ohm's Law: $I = V / R$
 $V = I * R$
 $R = V / I$

Voltage, current and resistance have a very close relationship and the interaction between them is governed by a strict law - Ohm's Law. This states that the current in a circuit is governed by the voltage applied to a circuit, divided by the resistance of the circuit, or $I = V / R$. But the same formula can be transposed so that where any two

factors are known, the third can be calculated. However it would be unusual to use Ohm's Law when diagnosing faults in automotive systems, I only mention it to show that voltage measurements can be used to 'see' the effects of unwanted resistance in faulty circuits and help to locate faults. Probably all wiring in a car will be copper which has a lower inherent resistance than most other metals. Steel or aluminium would be cheaper or lighter but have a higher inherent resistance, so would need to be thicker, taking up more space to compensate. Again, with only a couple of exceptions, the need for resistance measurements is rare in diagnosing electrical problems.


Watts or Power:

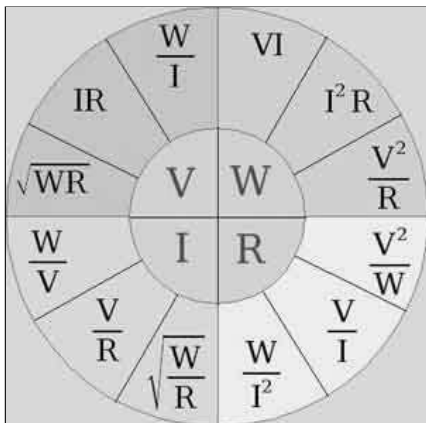

The Watt is the unit of power in electricity and is the product of Amps x Volts. About the only time you will see this used is in lighting and audio, and is an indication of how much energy a bulb - for example - consumes and how bright it is. For example if a headlight bulb is rated at 60 watts, on a 12 volt system, you can calculate the current that will flow by transposing the wattage formula i.e. Amps equals Watts divided by Volts, i.e. 60 / 12, or 5 Amps. When putting additional or more powerful lighting, audio or other systems on your car, this is the formula you should use to decide how thick the wiring needs to be. Other internet sources will give you guidance on what 'gauge' or thickness of wiring is needed for high power components.


Furthermore you can substitute the Ohm's Law formulae for voltage resistance and current into the wattage formula so that with any two values you can calculate the other two. For example to calculate the working resistance of a 60 watt bulb at 12 volts, use the lower right-hand quadrant of the calculation wheel, and the upper sector. Multiply the voltage by itself and divide by the wattage i.e. $12 * 12 / 60$ equals 2.4 ohms.

Earth or Ground:

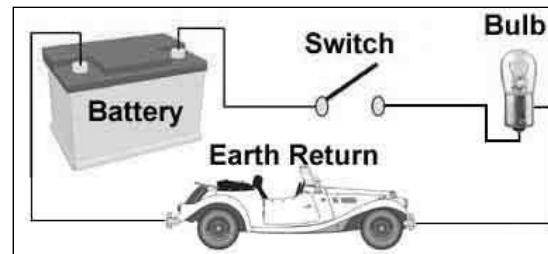


In practice and in all but very early vehicles 12 volts is supplied from the power source to one terminal of a component such as a light bulb, and another terminal of the component is connected to the car body. The other terminal of the battery is also connected to the car body, so it is the car body that completes the circuit to allow current to

return to the battery. This return path is known as the 'earth' or 'ground' return even though it has no electrical connection with the earth or ground the car is standing on (the terminology is historical). The car body is used as the return path as it is much cheaper and simpler than doubling up on much of the wiring in order to connect everything back to the battery. The car body itself offers a very low resistance return path, even though it is steel and not copper. Imagine the body was squashed as far as it could be both top to bottom and side to side, and rolled into a cylinder, but keeping the same length as the original car. How thick do think the resulting column of steel would be? I've no idea, but it's going to be several inches, thicker than the thickest cable on the car, which makes for a very easy path for the current to flow back to the source.

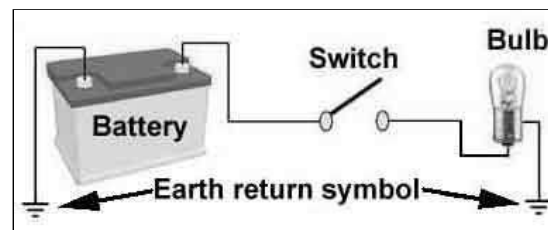

An earth return in circuit diagrams is usually depicted by the symbol shown here. All points in a circuit diagram with that symbol are effectively connected together, as if by wiring.

Live/12 volt and earth/ground terminals:

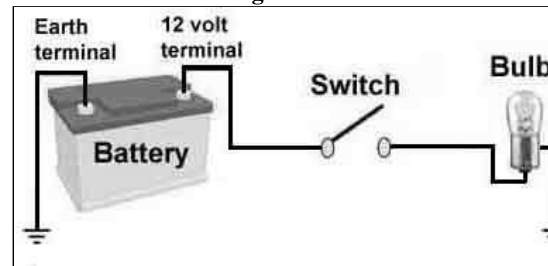

The live or 12v terminal feeds power to all the electrical circuits in the car, and its wiring must never be allowed to come into contact with the car body or severe damage can result (see 'Short-circuit' below).

The other terminal of the battery is connected to the car body and is the earth or ground terminal as described


above.

In the vast majority of classic automotive circuits power comes from the 'live' or 12v terminal of the power source, via wiring and switches to components, and from components it returns

directly via the car body to the battery to complete the circuit. In a few cases power is fed direct to a component, and the switch is in the earth return path.


Polarity:

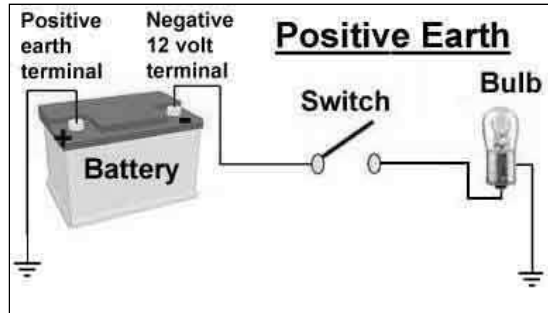One of the more confusing aspects with classic cars, especially to people who only have experience of 'modern' cars, and one of the most dangerous to get wrong. 'Polarity' refers to which terminal of the battery, positive or negative, is connected to the car body, and hence is the earth or ground return terminal.



Originally cars were wired for negative earth, then it changed to positive earth, then back to negative earth at various times. [The reasoning behind these changes can be found here.](#)

You have to be particularly careful with the MGB and maybe others of the same era as from inception to some point in 1967 the battery was wired for positive earth, but after that the negative terminal was connected to the body - negative earth or ground, which is probably how all modern cars are connected. However since leaving the factory some owners will have changed early cars from positive earth to negative earth for various reasons such as conversion from dynamo to alternator and for modern electronic accessories which can only be used with negative earth.

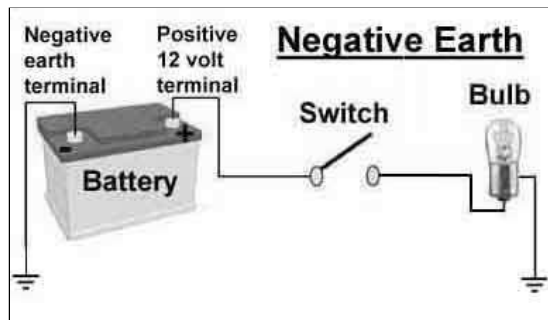

So if you are new to a particular car the first thing to establish is just what polarity it is, and that any labelling on the car and cable colouring at the battery reflects that. Note that the convention is that red cables or terminal covers indicate positive and black indicates negative. But usually on the MGB black are used for both and there are no terminal covers, which is why you need to be careful.


Note also that, regardless of polarity, power always comes from the live or 12 volt terminal of the battery, through wiring to components, and from components via the earth return back to the battery. In most cases the switch will be in the live wire between battery and component, but in a few cases it can be between the component and the earth return (e.g. early MGB wipers and most MGB horns).

Even more important is that if any stranger is to work on your car, and particularly if they are to use jump cables or a jump pack on your car, not only do they need to know the polarity of your car, but you also need to watch them like a hawk to ensure they connect them correctly. Incorrect connection can cause serious damage to wiring and components.

Also it is very important when you are going to work on battery connections, to always disconnect the earth terminal first, and reconnect it last. This is regardless of whether the battery is connected positive earth or negative earth. Ignore any instruction to remove the negative


terminal first, only ever the earth terminal, and that is regardless of polarity. The reasoning behind this is explained in the [detailed technical section on batteries.](#)

Open-circuit:

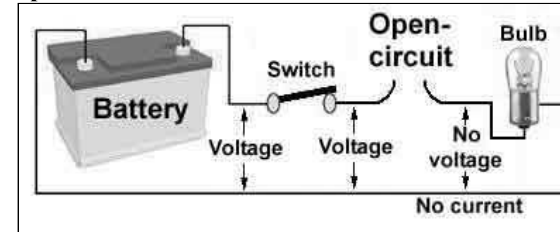


An open-circuit is where a fault has developed in a connection, component or wire that has either broken the circuit completely, or got to such a high resistance that there is effectively a complete break in the circuit as if a switch had been inserted, or a wire pulled off or cut. This is in addition to wires actually having fallen off components, or pulled out of connectors.

Short-circuit:

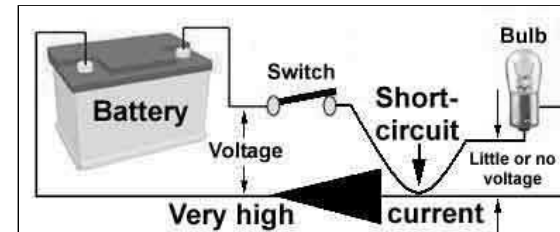

A short-circuit is the opposite of an open-circuit and is where a component has failed, or wiring has become damaged or has been connected incorrectly, such that much higher currents than normal can flow, and occurs when the current can find an 'easier' path back to the source than going through the component. It is called a short-circuit because the current is able to take a short-cut back to the source, and the very high currents that can flow can burn wiring and in extreme cases can destroy the car. Bear in mind that these very high currents flow in the whole of the circuit from the source, through the short-circuit and back to the source via any other components e.g. switches and connectors along the way, damaging those as well as wiring.

Fuse:

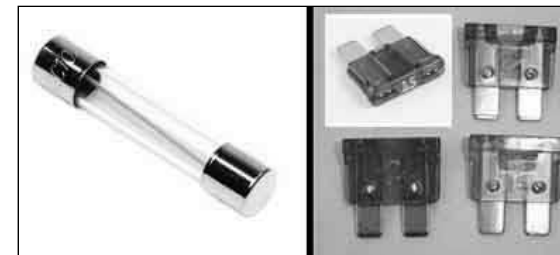


Fuses contain a short length of thin copper wire which 'blows' or melts to disconnect the power if the current through them exceeds a certain level. As mentioned above if a short-circuit fault develops very high currents can flow, and serious wiring damage can result.

But if there is a fuse between the power source and the fault then the fuse will blow to protect the wiring. Modern cars are almost completely protected against this type of fault with dozens of fuses, but the MGB and other cars of its era can have as little as two, which leaves a lot of wiring unprotected. Note that in classic cars, unlike most electronic equipment, fuses are there to protect wiring, not components.

The picture shows a typical original glass cylinder classic car fuse on the left, and modern 'blade' fuses on the right. The fuse 'rating' - the maximum continuous current it is designed to carry under normal conditions - is stamped into one of the end caps, or on slip of paper inside, or screen-printed on the glass of the classic fuse. Modern blade fuses by the colour off and legend

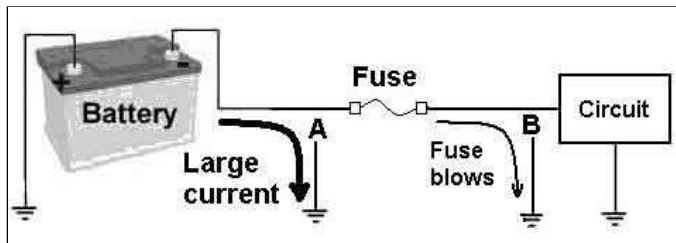on the top part. The 'fusing' current - the current at which the fuse 'blows' - is typically double the 'continuous' current in automotive fuses.




If you add fuses to circuits they need to be as near to the source of power as possible, not close to the component, in order to protect the greatest length of wiring. Consider a short-circuit to earth at 'A' above, and one at 'B'. At 'A' current will flow

from the battery to earth - a short-circuit - before it reaches the fuse, so the fuse is bypassed and it will not blow. In this case a very high current will flow and the wiring will burn. But with a short-circuit at 'B' current is flowing through the fuse and that will blow breaking the circuit and protecting the wiring.

You could have just one fuse in such a position that it protected all the wiring, but if that blew you would lose all the circuits on the car and have no idea where the fault has occurred. In practice where multiple fuses are fitted it is where wiring splits off to individual circuits, so only that circuit fails if the fuse blows, and the fuse that has blown indicates which circuit is at fault.

Series circuits:

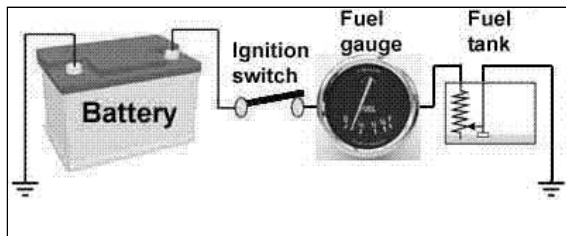


In the basic circuit above we have a simple series circuit of battery, switch and bulb, and this is the case for a number of circuits on a car such as where there is a single interior or luggage space light, and for the starter motor, the wiper motor, an electric fuel pump, where there is a single horn, and

others.

But some circuits have two or more components in series, as well as a switch and the power source. An example of this is the fuel gauge, where the power source feeds 12 volts through the ignition switch to the gauge, but instead of the other terminal on the gauge being connected to the earth return, it is connected to a variable resistance - the tank sender - inside the fuel tank, and the other side of the tank sender is connected to the earth return. As the fuel level in the tank goes down, for example, the resistance of the tank sender increases, which reduces the current flowing in the series circuit as we saw in the 'resistance' section above. This includes the fuel gauge, which is designed to move the pointer as the current changes, and so as the fuel level goes up and down the indication on the fuel gauge goes up and down.

Parallel circuits:

However many other circuits - mainly lighting circuits, have multiple bulbs like two headlights, four or more parking lights, two brake lights and also twin horns, and these are 'parallel' circuits. Where two or more bulbs etc. are required for a circuit it is normal to wire these in parallel with each other i.e. 12v is connected to one terminal on each of the components, and the other terminal of each component is connected to the earth return, so a separate current flows through each.

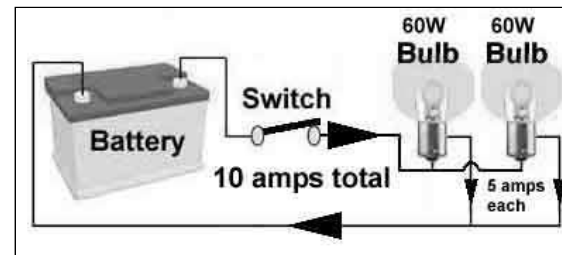

In the case of our 60 watt headlight bulb which took 5 amps, with two in parallel the total wattage and current in the circuit is doubled, i.e. 120 watts and 10 amps. Each bulb still only carries 5 amps, but the current from the source, through the switch, and through the wiring up to the point where it splits off to each bulb, is now 10 amps.

To do otherwise i.e. connect them in series would mean that if one bulb for example failed the other would stop working. Also from the 'bad resistance' example above you should be able to see that the voltage would be shared between the bulbs, so each of two bulbs in a circuit would need to be 6 volt bulbs. If there are four bulbs in circuit they would need to be 3 volt bulbs, and so on. Furthermore instead of the 12v supply being fed out to all the bulbs, and all the bulbs having their own earth return, each bulb in the circuit would need wire to get from one to the next, which would mean a lot more wiring.

Part 2 - further information on batteries; charging systems; the sort of faults that can develop; typical symptoms those faults produce; how to use voltage and to a lesser extent current and resistance measurements to detect and locate those faults and how to fix them [can be found here](#).



Automotive Electrics Basics

portions by Michael Beswick

If you find the information here useful, you may like to make a small contribution to help offset the costs of providing it. Thank you.



Last updated 15-Dec-2023

Part 2 - Electrical systems, typical faults, causes, symptoms, and diagnostic techniques

[Batteries](#) [Charging Systems](#) [Bad Connections](#) [Earthing/Grounding Points](#) [Test Equipment](#) [Voltage Tests](#) [Current Tests](#)
[Connectors and Terminals](#) [Using Circuit Diagrams](#)

[Click here](#) for Part 1 - Terminology

Batteries:


Car batteries contain a large amount of energy and can discharge it very rapidly under the wrong conditions, generating large sparks, toxic fumes, and even exploding showering corrosive liquid around. Not all batteries have polarity markings, on classic cars battery cables are not usually colour-coded for polarity, and the battery terminals and connectors do not usually have insulating covers. Great care must be taken to ensure the 'live' or 12 volt terminal does not accidentally contact the car body or a large spark can be generated which can ignite battery gases, and tools or other metal parts can become welded and glow red-hot.

Many MGBs and other classics of the era have two 6 volt batteries instead of a single 12 volt battery, and the two 6 volt batteries are connected together with a link cable. Both ends of this link cable must be considered as being 'live', as well as the 12 volt terminal, and need the same care to prevent accidental contact with the car body.

When doing any work involving any battery terminal, always disconnect the earth cable - the one that goes to the car body - from its battery post first, and reconnect it last. This is irrespective of whether your car is positive earth or negative earth, twin 6 volt batteries or single 12 volt battery. Many sources of automotive information say to always remove the negative connection first before the positive, but they are only thinking of 'modern' cars, not classics. I repeat, always remove the earth connection first and replace it last, regardless of polarity, and that applies to all cars i.e. moderns as well as classics.


It is absolutely vital that batteries are securely clamped into their cradles. Unsecured batteries have started fires in accidents, including [this horrific incident where the occupant was trapped and burnt alive](#).

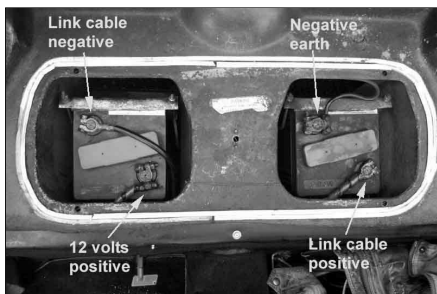The MGB along with most classics has a 12 volt electrical system, and has either one or two batteries under the battery cover on the shelf behind the seats.



Chrome bumper MGBs (and others of the era) originally had two 6 volt batteries connected in series with a link cable so as to deliver 12 volts.

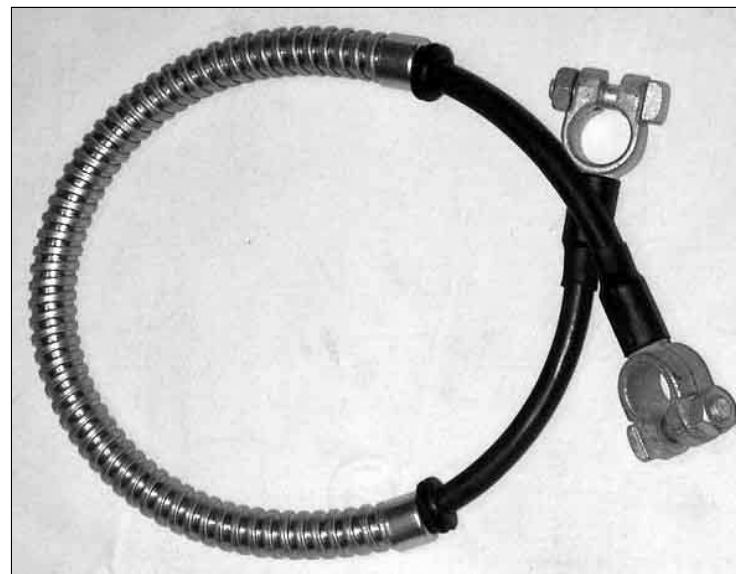To indicate polarity to others I've wrapped a strip of red plastic insulation - a spiral cut off a red battery cable - around the main cable that feeds power to all the circuits on the car, as well as round the positive end of the link cable.



Also shown is an armoured link cable available from various sources such as Motaclan/Leacy. This cable goes over the prop-shaft and it is essential that it is clipped to the back of the heel-board as high as possible. The armouring prevents the cable chafing in the clip, if this cable shorts out even though only one battery will be affected fire can still destroy the car.



Rubber bumper cars have a single 12 volt battery as shown here. This battery has a red protective cover over the 12 volt i.e. positive terminal and connector of the battery.

Some owners have modified chrome bumper cars replacing the two 6 volt batteries with a single 12 volt battery, usually for reasons of cost. However the 6v apertures and cradles are smaller and you end up with a lower capacity battery.

Battery capacity is given in 'cranking amps' - CA or 'cold cranking amps' - CCA. As the ability of a battery to deliver the high current used for starting reduces as the temperature reduces, the CCA figure gives a better idea of what a battery can deliver in winter, which is when most battery failures occur. Some suppliers use 'starting power' which is perhaps easier to comprehend. Battery capacity may also be specified as so many Ampere Hours, which is a measure of how long a battery can deliver a lower current such as for parking lights. More information on [these terms and how they apply to the MGB here](#).

Without going into the details of battery design and how they work, each battery consists of a number of 'cells' - three in each of the 6 volt batteries and six in the 12 volt battery. The only reason for mentioning this is that each cell contains a liquid consisting of acid and water, and the level of this in the cells must be right for the battery to work correctly. Again care needs to be taken as the acid can burn your eyes and skin and make holes in soft materials like seat covers and carpets, and can also be explosive. However under normal circumstances the only attention they need is to periodically have distilled or de-ionised water added to the cells, which in itself is perfectly safe to handle. Having said that most 12 volt batteries these days are 'sealed', and don't even need that attention.

Batteries can gradually lose charge on cars not used for long periods, particularly where things like stereo systems and alarms have been installed. This can be a particular problem on modern cars, where even two to four weeks can be enough to discharge a battery so that it cannot start the car. Easy enough to jump-start the car from a jump pack or another car, but great care needs to be taken particularly when using jump leads between two cars. Information on [safe use of jump leads can be found here](#).


To prevent this gradual discharge you can install a battery cut-off switch. These switches also act as an immobiliser, and can also prevent electrical faults causing damage while the vehicle is parked. I've witnessed a Transit van cranking itself across someone's front garden when a fault developed in the starter circuit. The switch - if accessible from the drivers seat - is also valuable as a safety device. There is much unfused wiring in classic cars, and in the event of a short-circuit on any of these wires much damage could ensue including total loss of the car to fire. Being able to stop the engine and switch off the power in seconds is far preferable to having to stop the car, get tools, access the battery, and disconnect the earth cable while wiring is burning. More [information on cut-off switches here](#).

Charging systems:

Even though the battery contains a large amount of energy it is a finite amount and when used to power circuits will eventually 'go flat' or discharge it all - just like a torch or flashlight battery - if it is not recharged or replaced. Continually replacing the car battery would be inconvenient not to say expensive, so there is charging circuit on the car that consists of either a dynamo or alternator, which under normal circumstances while the engine is running is continually recharging the battery - putting energy back in.

Although we talk about the MGB having a '12 volt' system a fully charged battery that isn't powering anything will actually measure close to 12.8v. If we now switch on some electrical circuits, its voltage will begin to drop, and a high power component such as the headlights will cause it to drop more and faster than, say, a low-power component like an interior light bulb. How much and how fast the voltage drops is also a factor of the power of a battery as well as how well charged it is - a weak or partially discharged battery, or a small capacity battery, will drop further and faster than a fully charged high-capacity battery.

In order to recharge a battery a voltage of greater than 12.8 volts is connected to its terminals, which is the purpose of the dynamo or alternator. This voltage has to be carefully controlled - too low a voltage won't recharge it properly and the battery will fail in a few months or weeks, and too high a voltage will damage the battery. The controller for a dynamo is called the 'control box', is mounted externally to the dynamo and typically recharges the battery with between 14 and 15.5 volts. This variation is due to the control box containing mechanical components which have adjustment tolerances as well as being sensitive to temperature. Alternators use an electronic voltage regulator which on all but the earliest versions is fitted inside the alternator body. It recharges with between 14.3 and 14.7 volts - not such a variation as the dynamo and its control box as there are no mechanical components to adjust and it varies less with changing temperature. These are the sort of voltages you should see on your electrical system, at various points, with the engine running at 2000 rpm or so, and it tells you your charging system is working correctly. **Never** run the engine without a battery being connected, high voltage pulses will be generated which can damage electronic systems and blow bulbs.

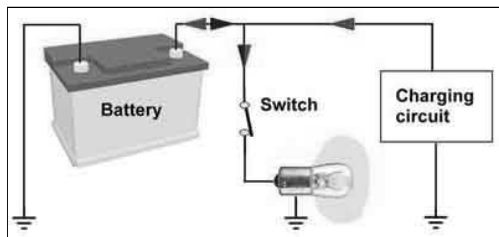

While the dynamo or alternator is outputting a voltage higher than the normal battery voltage it is charging the battery. Under these conditions when you turn on electrical circuits, it will be the dynamo or alternator that will be powering those circuits, as well as charging the battery (red arrows). So under normal circumstances, when you are driving the car it is the dynamo or alternator that is powering everything and not the battery.


However as with all things there are limits, and the limit here is how much current the dynamo or alternator is able to output. The dynamo used on the MGB can supply up to 22 amps, and the alternator can supply from 34 to 46 amps, depending on the year and model, later cars and the V8 having higher output alternators. Alternators on modern cars can supply up to a hundred amps or more as modern cars have so many more electrical circuits, some of them requiring a lot of power. The charging system doesn't suddenly 'switch off' if the current taken by your electrical circuits exceeds the maximum output available. What happens is that as the dynamo or alternator is asked to supply more and more current to electrical circuits, its output voltage and hence the voltage seen throughout the car will start to drop. As long as that voltage stays above 12.8 volts then it will still be powering everything as well as putting some charge back into the battery, albeit perhaps a very small amount. But if your electrical circuits start to take more than the charging system can provide, then the output voltage will fall below 12.8v, and at that point the battery starts to supply some of the current (blue arrows), and hence is discharging, despite the engine running. The more the current being taken by your circuits exceeds the output of your charging system, then the more the battery will be providing, and the further and faster it will be discharging. More information on [testing your charging system output here](#).

The other thing to bear in mind is that the output from charging systems is not constant but varies with engine speed i.e. how fast the dynamo or alternator is spinning. It goes up as the engine speed increases, to the maximum output currents indicated above - from manufacturers documentation typically 3000 rpm in the case of the dynamo and 6000 rpm in the case of the alternator. Below those speeds the maximum current that the charging system can supply may be less than quoted, so at low engine speeds your battery will begin to start supplying some of the electrical circuits and hence start to discharge with fewer things turned on, compared to when you are using high engine speeds. The alternator is less affected by this because of internal and external differences which means it usually spins faster than the dynamo at a given engine speed, and hence gives more of its output at lower engine speeds as well as having a higher peak output. An alternator should be charging well at idle - albeit not at its full output - even with several electrical circuits turned on, whereas a dynamo will only just be charging at idle and turning just one or two circuits on may be enough to start discharging it. This can be a problem for dynamo-equipped cars stuck in traffic on a winter's night with headlights, wipers, heater fan and perhaps brake lights on, but shouldn't be for alternator-equipped cars. Having said all that both systems should be charging satisfactorily under normal driving conditions i.e. 30mph upwards. There is [more information on dynamos and alternators here](#).


Even with a sound charging system batteries have a finite life, and the continual discharge during cranking and recharging during running gradually reduces their effectiveness. This is not usually seen as a drop in voltage as the car is being used, more likely over a period of years it will crank slower each time you go to start the engine. And if for any reason the engine doesn't start quickly the battery will 'go flat' sooner, i.e. lose all its charge and no longer be able to turn over the engine, compared to when the battery was new. This is most noticeable in cold weather, when the oil is thick, the engine harder to turn, and the battery finds it harder to deliver high currents. It's why a battery is more likely to fail in winter, particularly when there is a 'cold snap' or sudden spell of cold weather, which is a feature of the UK climate.

If you have flattened your battery, you may think that once the engine has been started e.g. with a jump-start your battery will be recharged over a period of time by the dynamo or alternator. Yes it will, but a battery that has become so discharged it is unable to start the car will only ever regain half its capacity from the vehicle's own charging system. Even a battery that has only lost 30% of its capacity will not regain all of it. The battery will work for a while, but it will fail to start the car again, under less arduous conditions than before, and you will probably come to the conclusion that it needs replacing. A new battery **will** solve the problem, but there are ways of charging batteries from external sources that will restore near full capacity, such as with a 'boost' charger or a 'conditioning' charger. A 'trickle' charger will not recover capacity as they output less than a dynamo or alternator. More information on [chargers and charging here](#).

Bad Connections

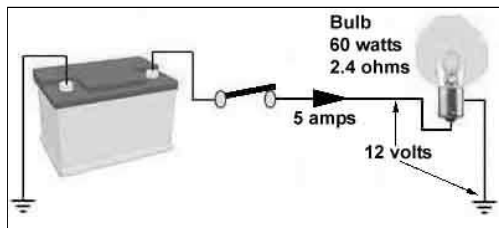

Bad connections add resistance to an electrical circuit, which reduces the current that can flow in a circuit, which reduces the voltage that reaches the component being powered. This results in dim bulbs, slow cranking, weak horns and so on. However there has to be some resistance in the circuit or an infinite current would flow, and you would need infinitely thick wiring to carry it. Taking the 12 volt, 60 watt headlamp bulb as an example and using the [Ohm's Law wheel](#) in Part 1 we can see that $R = V * V / W$ or $12 * 12 / 60$ which equals 2.4 ohms, that is 'good' resistance, and limits the current through that bulb to 5 amps.

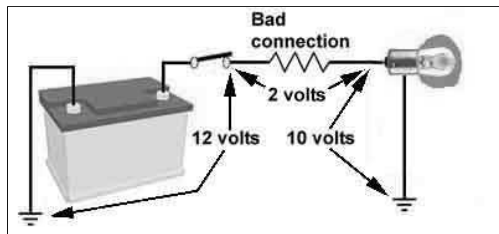

There is another source of resistance which comes from bad connections inside switches, where wires join components, or where wires join each other - this is bad resistance. Most circuits take a tortuous path to get a complete circuit from battery, through switch and component and back to the battery again, usually via many connection points. For example the indicator/turn circuit: Battery - battery cable - brown circuit - ignition switch - white circuit - No. 2 fuse - green circuit - hazard flasher switch - indicator flasher - indicator flasher switch - indicator lamp holder - indicator lamp - indicator lamp holder - earth - battery. And as well as all the item to item connections implied above there are also a number of in-line connectors in many of the interconnecting wires. In theory most components should receive the full 12v, but in practice every connector and length of wire imparts it own bit of resistance.

Straight out of the factory these additional resistances are minimal and for practical purposes can be ignored, but as our cars get older these additional resistances increase. As the resistances increase the current through the circuit reduces, and each of these additional resistances has part of the battery voltage 'lost' across it, which means that there is less voltage available for the end component. These bad connections build up over time from corrosion in connections caused by dampness and oxidation, and inside switches from the tiny spark that can occur when the contacts open to disconnect a circuit.

Take your stop lights which total 42 watts (two 21 watt bulbs in parallel) and draw about 3.5 amps from the 12 volt supply. Assume there is a bad connection between the voltage source and the component that happens to measure just 0.75 ohms. The lamps have a working resistance of about 3.4 ohms, and adding the bad connection becomes 4.1 ohms. The current is now $12 / 4.1$ or 2.9 amps i.e. less than the original 3.5 amps. Why does this matter? Use Ohm's Law again but this time transpose it to calculate the voltage lost in the bad connection i.e. 2.9 amps times 0.75 ohms which equals 2.1 volts. The significance of that is that there is now 2.1 volts less reaching the stop lamps, i.e. slightly less than 10 volts, so they won't be as bright as they should be, which is the last thing you want from classic car lighting.

A reduction in brightness is bad enough, but the flasher units used in cars of this era are very sensitive to reduced current, causing a slower flashing rate or not flashing at all, and it can be a time-consuming process tracking down small amounts of unwanted resistance in the many connection points of this circuit. There is more information on [diagnosing faults in the indicator/turn signal circuit here](#).

However this feature of electrical circuits with bad connections - different voltages at various points along a circuit - means that by measuring voltage in circuits that aren't working as they should, you will be able see if it is bad connections that are causing the problem. Even more importantly the 'lost' voltage can also be measured with your test meter, and this can be used to find exactly where the bad connections are. This is probably the single most important thing to understand when diagnosing faulty circuits.

But going back to 'good' resistance, whilst we can use the wattage of a bulb to calculate its resistance, it is important to realise that is the **working** resistance when the bulb is glowing at full brilliance i.e. white-

hot. When the bulb is off and cold it exhibits a much lower resistance on a test meter - a 60 watt headlamp bulb for example measures only 0.1 ohms when cold. This effect - of resistance increasing with heat - is called the 'positive temperature coefficient' of a conductor, and means that when first switched on bulbs take a high current until the filament has heated up. This is a major cause of failure in replacement brake light switches. More information on [brake lights and switches here](#).

Motors also take less current when running normally than the resistance shown by a test meter would indicate. In the case of the heater fan motor the measured current is about 4 amps, which implies a resistance of 3 ohms. But measuring the resistance with the motor stationary displays about 1.5 ohms, which would imply a current of about 8 amps. Again that is due to a physical characteristic of motors - in this case 'back-emf' which is where a spinning motor generates a voltage in opposition to the supply voltage, which reduces the current the motor takes. This also results in the initial switch-on current being significantly higher than the running current i.e. once the motor has got up to speed. But if the motor is seized or otherwise jammed the higher current will flow all the time, and the heat generated usually causes the motor to burn out, which can extend to catching fire and spreading to the rest of the car. Incidentally, this 'back-emf' is also generated when the motor is being spun by mechanical means, which is basically how a dynamo works.

Other than the specific issues with brake light switches and stalled motors I only mention these factors to show that taking resistance measurements on circuits when looking for faults can be misleading.

Bad connections have bad habits: When current flows through any resistance it generates heat, which is why light bulbs get hot when they are glowing, for example. The same happens where current is flowing through a bad connection, these can heat up as well, which is one reason why switches and connectors can melt even without a short-circuit fault. This leads to another very important thing to understand when diagnosing electrical faults. Bad connections are almost always variable in their nature, with variations in resistance and hence current and 'lost' voltage in them being caused by vibration and heat. There is inherently significant vibration in a car, and considerable temperature variation in the engine compartment between just started and fully up to temperature as well as anywhere on the car between seasons. So with bad connections generating heat, and heat and vibration causing bad connections to vary, fault symptoms become variable and the causes difficult to track down.

If you pull wiring around and waggle connections you can alter the resistance of the bad connection, which may cause the symptoms to get worse, or indeed the fault may go away - for a while. Sometimes this can help you find the location of a fault but it's not reliable, and can be confusing. Wiggling a bad connection may well make the fault go away, but unless you open up the connection and clean, tighten if loose, or replace the parts if heavily corroded it is bound to return. Components themselves can develop internal weak connections which vary when they get hot causing the component to fail, a known failure mode of some ignition coils for example. Ignition coils do heat up in use, that in itself doesn't necessarily indicate a fault, but there are limits. More information on [hot coils here](#).

Similarly because heat can cause a bad connection to vary, measuring resistance to look for bad connections is unreliable. In almost every case the current in a circuit from a test meter measuring resistance will be microscopic compared to the current that would normally be flowing. Heat from normal current could well be causing the bad connection to change and hence a fault to become apparent, but when measuring resistance with a test meter there won't be any heat in the bad connection, so it is quite likely to react differently, and what your test meter will be telling you is not the same as what the circuit itself will be telling you when powered normally - more confusion.

But the opposite side of that particular coin concerns switches. These mostly have brass or silver contacts which can develop a thin film of oxide when not used for a while. Test these with an ohm meter and you may well see some resistance and think the switch is faulty. But that's because the tiny current from the meter cannot fully break down the oxide. Apply normal circuit conditions to the switch and measure the voltage between its closed contacts, and you will most likely see little or no voltage lost in the switch. This is because under normal working conditions the 12v system voltage will break down minor oxidation, and allow a normal current to flow. An exception to this is the standard fuel pump, where the contact points have oxidised during storage or a long period of not being used. Only mechanical abrasion

will clean off the oxidation, and new pumps contain a slip of paper to this effect and ask you to clean the contacts before returning the pump as faulty. More [information on diagnosing the fuel pump here](#).

For all these reasons the only reliable indication of bad connections, and where they are, is by measuring voltages when the circuit is connected and powered 'normally'.

The wiring in car systems is almost always copper as copper has a lower resistance to the passage of current than other metals such as steel (which would be cheaper) or aluminium (which would be lighter). But even copper wires have a certain amount of resistance, and so will heat up when a current is passed through them. When designing an electrical system the amount of current that the wire will be required to carry is taken into account when deciding how thick the wire needs to be - just like in house wiring cabling for power sockets is thicker than for lighting circuits. The result is that under normal circumstances you won't detect any rise in temperature in a wire. Where factory wiring does heat up and burns the insulation the reason will always be that there is a short-circuit fault somewhere causing a much higher current than anticipated to flow in the circuit. Note that this can also happen with owner modifications where wire of too small a gauge (thickness) has been used to connect a high power component like a powerful lighting or audio system, or the wiring has been done incorrectly and caused a short-circuit. Most circuits in an MGB don't take more than about 5 amps. A pair of headlights takes about 10 amps, but this can double to 20 amps if you should happen to operate your headlamp flasher while your dipped beams are on, and is why headlamp wiring is normally thicker than most other wiring. However the starter takes about 200 amps as a lot of energy is required to spin the engine, which is why the cables to the battery terminals, the starter solenoid and the starter, and the engine or gearbox earth strap, are as thick as they are.


Earthing points:

As seen in [Part 1](#) all circuits use the 'earth return' i.e. the car body so current can get back to the battery. Everywhere a component, including the battery, is bolted to the body corrosion can occur, making bad connections. And being steel this is much more likely and to a worse degree than corrosion in electrical components which are usually copper and brass. As a result bad earths are a common source of electrical problems in a classic car.

There is also the complication that not every component has its own earth connection to the body, in most cases several are joined together in wiring first, then one or several wires will be connected to the body at one of the earthing points. If one of these earthing points develops a bad connection then the circuits connected to it can interact in apparently weird and confusing ways.

There are typically only three wired earthing points to the body in an MGB - in the engine compartment, behind the dash and in the boot, plus the two most important - at the battery without which nothing will work, and at the engine or gearbox. This latter is a wide braided strap for flexibility as the engine moves on its rubber mounting points during use. If this strap fails the engine will either crank slowly or not at all as it is the return path for the 200 amp cranking current. However the starter circuit is like any other circuit in that its current will try to get back to the battery any way it can. There are several other metallic connections between engine and body such as the heater, choke and accelerator cables and the temperature gauge capillary tube and speedo cable. With a bad engine or gearbox earthing strap these can all get very hot during cranking and indeed suffer damage.

A few components are bolted directly to the body and make their earth return connections that way. Tail light assemblies with three circuits sharing a common earth can be particularly difficult as one bulb circuit will try to earth through another circuit if a shared earth is poor. Various lights will flash on and off or go dim and bright when they shouldn't when two or more circuits are powered at the same time - known as "disco-ing" in MOT circles. Each bulb earths to its bulb holder, the bulb holder to the light unit base, and the light unit base to the car body. If the bad connection is between the bulb and its holder, then in the case of the stop/tail bulbs the stop and the tail lights will interact, but the indicator bulb will work correctly. But if the bad connection is between the light unit base and the car body, then all three lights will interact. This discoing can extend to the other corners of the car from the faulty corner, even though the circuits are, on the face of it, separate, and there is nothing wrong with the connections at the other

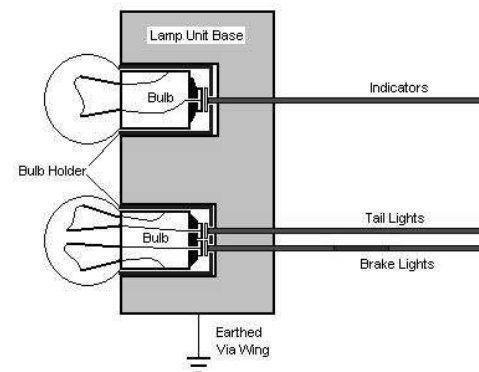


corners. Current in any circuit with a bad shared earth will try to get back to the battery any way it can, including back up the wires and through components of the other circuits affected by the same earthing fault.

A quick simple test is to add a temporary earth; If adding an earth between the tail light assembly and a good earthing point solves the problem, then the fault is the connection between the light unit and the body. If it does nothing, then the fault is either with the bulb or bulb holder, and there have been instances where the bulb holder is making a poor connection to the light unit base.

Chrome-bumper front parking/indicator assemblies i.e. two circuits are the same in that they earth through their physical fixings to the wings. Rubber-bumper front indicator units have an earth wire going to the cluster in the air intake by each headlight, but in any case only have one circuit. Another problem area is the earthing of the bumper-mounted number-plate lights, which is also through their physical mountings.

See also these thoughts from Felix Weschitz on [getting good earth connections](#). Additionally I always daub Waxoyl on all nuts and bolts, whether on the body or not, electrical connections or not, to delay the onset of the dreaded corrosion particularly where things are bolted to the body and where the paint is inevitably damaged.

Test equipment:

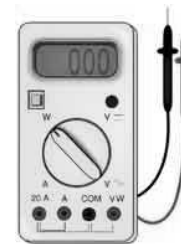


In order to measure voltage, current and resistance you need a multimeter. Cheap home-use meters will be able to measure all three, more sophisticated and expensive versions will measure other automotive parameters such as engine revolutions per minute (rpm) and ignition characteristics. Most these days will have digital displays, older instruments will be analogue i.e. with a pointer physically moving across a printed scale. After you purchase one, read the instructions and practice measuring voltages and resistances with it, and there are strict Do's and Don'ts to be observed when using one.

- A meter is an electrical component and as such has an inherent resistance like any other electrical component. When used as a voltmeter the instrument has a very high resistance in the hundreds of thousands of ohms or higher. This means a voltmeter can safely be connected to the terminals of a battery, or between any two points in the electrical system (except the ignition HT (High Tension) leads), as with a resistance that high only a microscopic current can flow.
- However the same cannot be said when the test meter is used as an ammeter. This measures current by being inserted into the circuit such that all the current flowing in the circuit flows through the meter as well. For that reason an ammeter has a very low resistance - a fraction of an ohm. If it had a high resistance it would significantly affect the operation of the circuit you were testing - not much help when you are trying to diagnose a fault. For that reason you must **never** connect an ammeter between a 'live' wire carrying 12 volts and earth. If you do, you will have created a short-circuit, and a very high current will try to flow. Most multi-meters with a current function should have a fuse, which will blow as a safety feature to protect both the meter and any circuit it is connected to. If not you will damage both meter and car wiring. Once this fuse blows the meter will probably work on voltage and resistance, but not for current, which can lead to more confusion. There is really only one occasion when use of an ammeter is required, and that is when testing the [later overdrive circuit](#).

- Similar care needs to be taken when measuring resistance. For this a low-voltage battery inside the meter is used to drive a small current through the component or circuit being tested, and the level of the current together with the known voltage of the internal battery allows the meter to calculate and display the resistance. Resistance measurements cannot be taken on a component or circuit that is powered from another voltage source, the two voltages will conflict and you will get confusing readings. You may also damage the meter if it is connected between a 12 volt supply and an earth. There are very few situations where a resistance measurement might be required on the MGB - one is to measure the resistance of the [overdrive solenoid](#) if a current reading is lower than expected, or the primary winding of the [ignition coil](#), or perhaps a [relay winding](#), or maybe a continuity test of a light bulb. In all other cases voltage measurements should tell you all you need to know.

Okay, you've been wandering around Halfords and whilst picking up other things bought yourself a shiny little electrical test meter. You fitted the battery maybe even read the instructions and it's now sitting in the garage until you need it.

Before you actually start to use it, it's worth examining it quite closely. Firstly the leads are too short, they are covered in plastic, and as you always do this the middle of winter, the lead are stiff when cold and pulling on them always causes the meter to fall off whatever you put it on. The second problem is that in almost every case you will need to have one of the meter leads attached to a Good Earth. How do you find one of those? By connecting the meter between one point that should have 12v, like the brown at the fusebox, and the earth you are proposing to use for your tests. If the meter shows 12v then you can proceed. If it doesn't, then either your earth is no good, or your 12v point is no good, or maybe both are no good (or maybe your meter is no good...). So try other points until the meter shows 12v. At this point you wish you had bought a package of ancillary leads that included crocodile clips (which cost as much as the meter..)

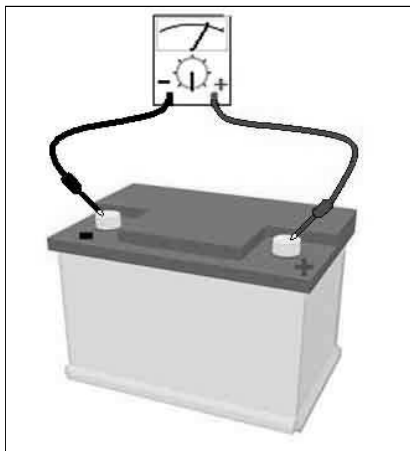

As in the image above meters usually have at least one red socket for the positive probe, and at least one black socket for the negative probe, and there may be others, for various test functions. Usually either lead will physically fit either socket, but of course the convention is to plug each lead into the same colour socket.

When measuring voltage and current with an analogue meter the probes need to be connected to the circuit 'the right way round', that is with the red or positive probe connected to the point in the circuit that is positive with respect to where you will position the black or negative probe. In general what this means is that if your car has the batteries connected for positive earth, then usually the black probe of the meter needs to be connected to the terminal or wire being tested, and the red probe to a convenient earth. If your car has the batteries connected for negative earth then the red probe will go to the wire or

terminal being tested and the black to a convenient earth. If you get the probes the wrong way round the needle will try to move backwards, although this is very unlikely to damage the meter. Most if not all digital instruments will display the voltage or current no matter which way round the probes are connected, although if you have the probes the wrong way round they will usually display a minus sign '-' in front of the numbers.

For most of us we will only ever use the 12 V DC range. About the only time you would use an ohmmeter is when you are testing a component for continuity such as a fuse, a bulb, a relay or solenoid winding. But even those, and particularly a fuse, can show continuity with an ohmmeter, but go open-circuit when a larger current is drawn. So for problems on circuits where the fuse shows continuity, you will have to go back to using the voltmeter or test-lamp both sides of the fuse and fusebox while the

circuit is being powered and drawing (or trying to draw) current. More [information on fuses and fuseboxes here](#).

It is sometimes necessary to check a wire itself. The meter probes usually have sharp points to push through the insulation and make contact with the wire. They also have a habit of making contact with your fingers. To avoid this, find a small block of wood or plywood; file a 2-3mm groove along its length. Drill a 2-3mm hole mid way along the groove. Now by placing the wire in the groove you can pierce the wire and not your fingers. Sometimes it may be necessary to make a semi permanent connection. A domestic pin or similar can be forced through the insulation and wire exiting through the hole. Then a croc clip can be attached to the pin. Remember that, depending on the use of the wire the pin may become "live". Much wiring is unfused, but pretty-well all wiring will carry 12v at some point in time. Be careful that your test clips etc., do not bridge wires or connections to other metal parts, which might be at earth potential, which can damage the wiring.



One of the first difficulties is that different faults require different types of measuring kit. Sometimes there is an overlap and in most cases a test-light will work as well as a meter. This is a small 12 volt bulb or LED, inside a probe similar to a screwdriver, with a point at one end and a wire with a crocodile clip at the other. Or it could simply be a spare bulb with two bits of wire soldered to it. The crocodile clip is put on a convenient earth point, and the probe placed on another connection or terminal point. If there is 12 volts present at the connection or terminal the bulb or LED will glow, if not it won't. It can also be used to

check for an earth, by putting the crocodile clip on a convenient 12 volt source such as at the fuse box. Always check the test-light first by putting the probe on a known source of whatever it is you are looking for, much time has been wasted looking for a broken connection when it has been the crocodile clip on a poor earth or the test light that is broken. For example, when looking for 12 volts, the crocodile clip will be on a convenient earth point, so touch the probe to, for example, the brown wire terminals of the fusebox, as these should have 12 volts all the time. When looking for an earth and the crocodile clip is connected to a 12 volt source, touch the probe on a convenient earth point such as somewhere on the engine.


In other cases such as an indicator/turn-signal fault where they light but don't flash, test-lights are not sufficiently accurate (how can you tell how bright or dim the bulb is...), which is when you need a meter as voltage drops small enough to affect the circuit may not be seen on the test-light. There is more information about diagnosing [slow or non-flashing indicators here](#).

Horns are another circuit where a small drop in voltage to the horns causes a significant reduction in sound output and where a voltmeter is preferable for diagnosis. More information of [diagnosing poor horn output here](#).

There is only one type of diagnosis where a particular type of 'test-lamp' is preferable to a meter, and that is if you have a continually blowing fuse. You use a high-wattage bulb in place of the fuse - purely during diagnosis - and when the short is present it glows at full brilliance and when the short isn't present it glows dimly or not at all. More information on [diagnosing blowing fuses here](#).

Voltage tests:

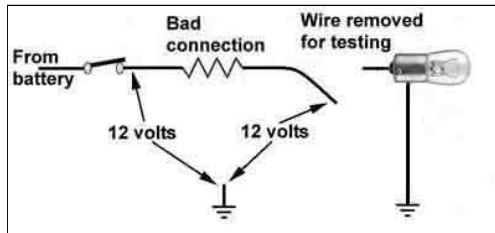
The most important thing to remember when making tests with either device, is that the circuit must be fully connected and powered 'normally' in order to give useful results, and this all goes back to resistance - the natural working resistances of components on the car, and the inherent resistances of the test meter and test-lamp.



Remember our volt-meter has an inherent resistance of hundreds of thousands of ohms, however probably every component in the car will have a resistance of less than 10 ohms. If a component isn't working so you remove a wire from it and test the wire for 12 volts, you may well see 12 volts displayed. But when you connect 12 volts from another source via a temporary wire to the same component, the

component works! How can this be? It's all to do with relative resistances in a series circuit. If the normal circuit for the component has a bad connection measuring, say, 1 ohm between the 12 volt source and where you test with your meter, then your meter will display 12 volts. This is because the resistance of the meter is so high, which means the current drawn by it is so low (in the order of millionths of an amp) that there is only a microscopic voltage 'lost' in the bad connection, so effectively all the 12v volts is still available for the meter to display. But when the wire is connected to the component a much higher current will flow, and much more voltage will be 'lost' in the bad connection, so the component cannot work correctly.

For that reason the wire being tested must be connected to its component, **and** the circuit powered as it normally would be, **and** the fault must be present when you take your voltage measurement, in order for the meter to show 'lost' voltage. Fortunately most connectors and component terminals on the MGB are 'open' and can be tested with a probe while assembled. Modern wiring has sealed connectors and terminals, which keeps out the damp and corrosion that plagues classics, but also prevents access for testing.

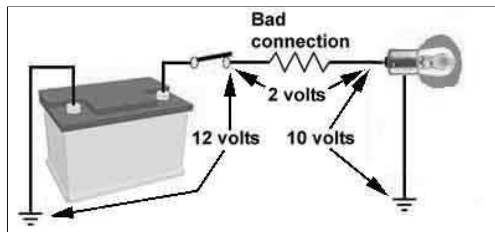


In our example with a bad connection between switch and component, if you connect your test meter between the output from the switch and earth, you will probably see 12 volts. But if you now test the other end of that wire when it is on the component you will see less than 12 volts. The difference between what you see here and 12 volts is what is being 'lost' in the bad connection. There is another way of testing for

lost voltage and that is to connect one side of your meter to the output terminal of the switch, and the other side of your meter to the input terminal on the component. If there is a bad connection between the two then you will read the lost voltage directly. But the component must be connected and powered for these tests to be useful.

A meter will give you the exact voltages in a circuit, but a test lamp can be used to give an indication. However it does depend on the voltage differences being large enough to cause the test lamp to give different indications, usually as a change in brightness, and that is very dependant on the type of test lamp being used. LED test lamps in particular may need quite a large voltage difference before they give a detectable difference in brightness. Test lamps are most useful when a component isn't working at all i.e. there is an open-circuit or the bad connection is so bad that little if any voltage is reaching a component. A meter will show you tenths or even hundredths of a volt difference between two points, but by the same token don't make the mistake of trying to track down and eliminate every last tenth of a volt.

As stated above small bad connections have a disproportionately large effect on the starter circuit because of the very large currents flowing. For example, using Ohm's Law, a 0.05 ohm i.e. five hundredths of an ohm bad connection in the headlight circuit will reduce the voltage at the headlights from 12 volts to 11.6 volts - not that much. But in the starter circuit that same resistance will reduce the voltage at the starter to 6.5 volts i.e. almost half! In fact it will be lower than that, as even the best car battery can't maintain 12 volts while cranking an engine. In practice the voltage at the terminal posts of a sound battery will drop to about 10 volts while cranking, and this is the voltage you should be using as the comparison when making voltage measurements elsewhere in the cranking circuit.

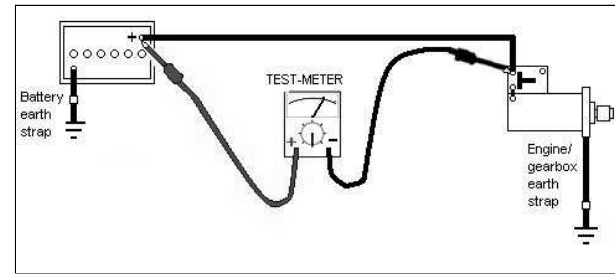


I have seen 3 volts 'lost' in battery cable and starter connections but the engine still cranked - albeit slowly - and started. Anything more than 1 volt is worth investigating, and you should be able to get it below 0.5 volts in total i.e. what is lost in the 12v cable and connections and the earth return connections. An important thing to note about bad

connections in the cranking circuit is that in most cases these will result in reduced voltage to the ignition system as well, making starting even harder. There is more information on [starter problems here](#).

There is one circumstance where you use a voltmeter, but connected like an ammeter i.e. in series with a circuit, and that is when you are investigating why the battery seems to be going flat while the car is parked, i.e. while everything is supposed to be switched off, aka 'battery drain'. More information on [diagnosing battery drain here](#).

Current tests:

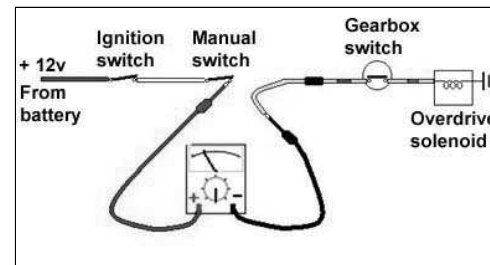

Very occasionally it may be necessary to measure currents such as when diagnosing the overdrive circuit. If the overdrive isn't operating, then the problem could be electrical, mechanical, or hydraulic. The first thing to do is to see if it is an electrical problem, as they are almost certainly going to be easier to resolve than hydraulic or mechanical problems.

You could use a voltmeter or a test-lamp, testing at various points along the circuit, but neither

are going to indicate a problem if the fault is a broken OD solenoid winding or if there is a bad earth at the solenoid, meaning no current is flowing. Also to get at some of the connections for voltage measurements you will have to grovel under the car.


You could use an ohmmeter and measure the resistance of the solenoid winding to earth from a convenient point at the manual switch or gearbox harness bullet connector, but as already stated bad connections by their very nature can give variable resistance readings. An ohmmeter may show a good circuit, but a bad connection may be breaking down when the full current tries to flow.

The only way to get a reliable indication that the OD solenoid circuit is working as it should - electrically speaking, is to use an ammeter, with the ignition on, manual switch operated, and the gearbox in an overdrive gear. That way, the circuit is being operated in its normal way, and any problem causing insufficient current to flow (or too much from a partially short-circuit winding or wiring) will immediately be shown on the ammeter. It also means only one test is needed to prove the problem is or isn't electrical, which can be done from a convenient point at a manual switch or connector.

Remember that an ammeter will only show whether the current in a circuit is correct or not, it won't help you determine where any faults are, no matter where you connect it. Also remember that analogue meters must be connected the right way round to correctly display current, the same as for voltage. The above example shows how to connect the meter for a negative earth system, i.e. where the 12v supply is positive with respect to earth. If no or insufficient current is flowing, **then** you will need to test the voltage at each of the points in the circuit to try and find out where the break or bad connection is. If you see 12 volts all the way to the connector on the wire that comes out of the solenoid, then the problem must be with the solenoid or its earthing. However there are only a couple of circuits where current is a

useful diagnostic measure, click the links for more information on [diagnosing overdrive electrical problems](#) and [ignition coil problems](#).

Connectors and Terminals:

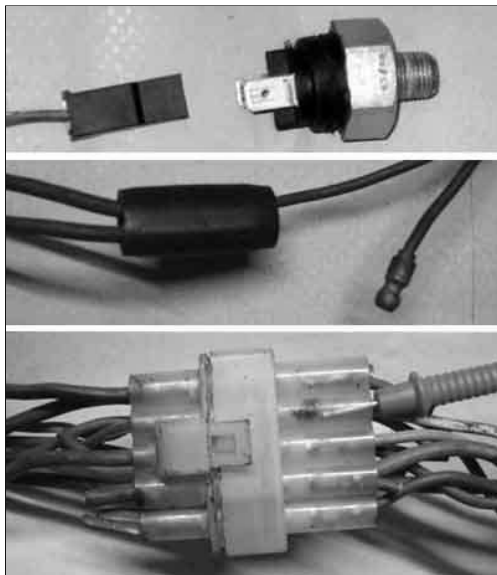

When checking voltages at components check the component terminal i.e. its spade as well as the terminal on the end of the wire that slides onto the spade as corrosion can develop between the two. Factory wires are usually spot-welded to the spade connectors so pretty robust and the least likely to fail.

Test the voltage on each side of bullet connectors as either bullet could be making a poor connection with the connector sleeve. Bullets are crimped onto the wires in factory harnesses, usually OK, but at the front of the car you can get corrosion running under the insulation for several inches. In one case I've had the conductor strands corrode right through where the insulation was damaged on an unsheathed headlight wire under the wing.

Translucent multi-plugs such as these can have probes pushed in from the rear, however black and grey multiplugs are usually moulded onto the wires and pins and cannot be tested in this


way.

Aftermarket modifications and repairs using crimp terminals often cause problems.

In all cases the connections must be together, not parted, or you will get incorrect results. More information on [Connectors and Terminals here](#).


Using circuit diagrams:

Before you start diagnosing a circuit, you need the correct wiring diagram to identify which is the relevant wire (by colour code) and terminal on switches and other components. It's important to get the right diagram for your model and year, as there were many significant changes throughout production, leading to at least 25 circuit diagrams for the MGB plus a few supplementaries. That's in the Leyland Workshop Manual, Haynes condenses these down into just 9 by combining several lesser changes in successive years into a single diagram. But by only showing one of several possible wiring situations for a particular circuit the Haynes diagrams can be confusing. The Leyland (workshop manual and glovebox handbook) and Haynes diagrams can be difficult to follow as generally they position components as they would be on the car, which results in many wires snaking all over the place.

As an alternative you can use either the [individual circuit elements as here](#) , or these [Advance Autowire diagrams](#) which although showing all the circuits for a particular model in one diagram, has the components grouped together by function which results in much less wiring.

However one major benefit of the original Leyland diagrams is that they show all the junction points for wiring and common earthing points, which are essential where the problem is one of strange interactions, rather than simply a circuit not working. Even in the latter case knowing how the 12 volt supply splits or branches off to components, and which are working and which are not, is very helpful in determining the likely location of a break in a circuit before you start, which can greatly reduce the number of points you have to test, as in the following example.

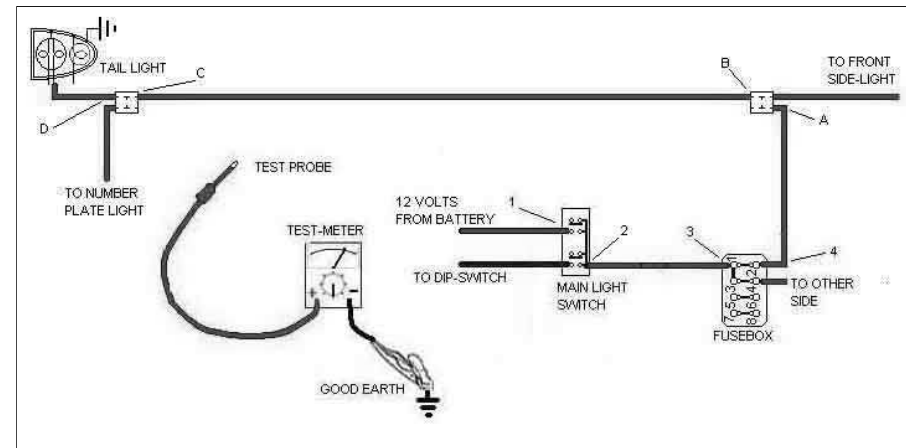In this example the non-working component is a tail light bulb, so we need the correct wire, fuse and switch terminals for the sidelight circuit - in this case a 1970 and later model i.e. negative earth so a positive 12 volt supply - where ABCD are bullet or other type connectors.



With meter on the 12v range, the negative black lead attached to a known good earth (for a negative earth car, reverse for a positive earth), you will touch the other (+ve) probe to any connectors to the switch, then each of the Light Switch terminals, to each end of the fuse, then ABCD in turn. The circuit must be "on" to try this, even if the component - the bulb - is not working as it should.

1. Put the probe on the inward terminal of the switch wire probably brown. If not good or a large drop, there is a fault in the wiring from the solenoid to the switch. This is a key circuit: the terminal on the solenoid is directly connected to the battery. If the fault is between the solenoid and the battery (unlikely) there are other major faults. The brown wire from the solenoid feeds several things within the harness - one of which is the head and sidelight switch.
2. If there is no reading on the correct (sidelight) outwards terminal of the switch, then the switch is faulty. But this only is true if test 1 has been completed to eliminate the faults described.
3. Test the input side of the fuse box
4. Test on the outward side of the fuse box
5. Test each connector A B C in turn. All OK?
6. Test at D - if there is a zero reading this indicates the fault lies between C and D. If the reading is lower than that obtained at C there is still a fault between C and D but it is not a simple break - more likely a corroded terminal.
7. So you've guessed it - you have to check both "ends" of bullet connectors (even then the contact between a bullet and its sleeve can be bad) and between any spade connectors (female) and the lugs (male).
8. There may be a steady small reduction in the readings as you approach the component. In most cases this is OK, if it is bad enough then the component will not perform as it should. (A case in point is indicator circuits. There are 23 different connectors between the fuse box and the bulb all of which can drop a little voltage. In each case a little resistance is added to the circuit. This added resistance reduces the ability for current to flow. Where the current is insufficient it will not operate the "flasher unit" but will still light the bulbs to what seems to be full brightness).
9. Remember that the component itself (in the case of a bulb,) can have poor connections. Usually caused by years of moisture corroding the contacts.
10. So now you have tested right up to the lead that connects to the component itself: still you have 12v. But still the component does not work!
11. If the component has a lead from it running to earth (usually black) test at this point. If there is still about 12v the component is OK. Your problem is a poor/bad earth.
12. Many components earth through their fitting to the body. This can be poor but can be resolved by cleaning or fitting an "extra" lead to a separate earth.

But! If the front parking light is working, then there must be voltage at point A at least. Also that if the associated number plate light is working, then there must be voltage at point C at least. It's logical deductions like these, from looking at what works and what doesn't together with the Leyland diagrams, that can save you a lot of testing time, and in many cases lead you right to the fault. In this case it depends on whether the tail light doesn't work at all, or if it 'discos' with the brake and indicator lights. If it doesn't work at all then it must be where wire D plugs into the bullet connector, where that wire connects to the bulb contact in the bulb holder, or the bulb filament is blown. If it is discoing with the brake light **and** indicator it must be the earthing of the rear light unit to the wing. If the discoing is only with the brake light i.e. the tail light goes out that side and the brake light doesn't come on when you press the foot brake, then it must be the earthing of the bulb or bulb holder.

And perhaps the most important thing to bear in mind is that just because you have found one fault, don't assume that is the **only** fault. In other words if you have one corroded connector causing a high-resistance joint, you could well have several, particularly at the front of the car behind the grille where they are exposed to the worst of the weather.